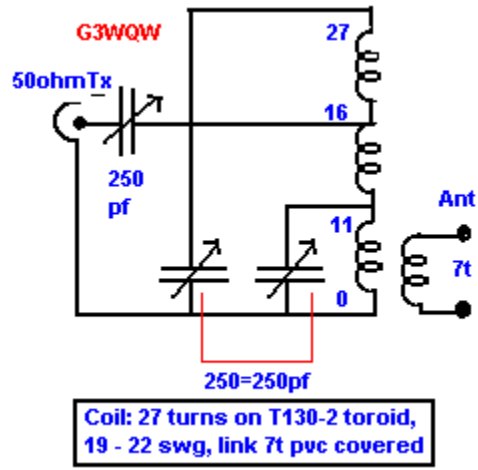


A SINGLE COIL Z-MATCH



This ATU was described by **G3WQW** in Sprat 84 and being balanced can accomodate balanced line, open wire feeder or 300 ohm slotted.

250pF polyvaricon capacitors can be used for up to 15 watts, and a T130-2 toroid. Wire can be 1mm (19 swg) to 0.71mm (22swg), readily available from electric motor repairers etc.

A very useful circuit for the QRPer.

Frank, G3YCC